

Date: 09.04.2019

Student Names: Salih Can Özçelik / Muhammed Halas

Student IDs: 2016400207 / 2016400228

Group ID: 6

Session ID: 2

CMPE 240 Experiment 5 Preliminary Work


1. State Register Inputs: Clock, next state ($d1, d0$)
2. State Register Outputs: current state ($n1, n0$),
3. Combinational Block Inputs: X , current state ($n1, n0$)
4. Combinational Block Outputs: next state ($d1, d0$), outputs($y1, y0$)
5. Obtain the truth table.

$n1$	$n0$	X	$d1$	$d0$	$y1$	$y0$
0	0	0	1	0	1	0
0	0	1	0	0	1	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
1	0	0	1	0	1	0
1	0	1	1	1	1	0
1	1	0	1	0	1	1
1	1	1	1	1	0	1

6. Is this a Moore or Mealy Machine? (No explanation, only short answer)

Mealy Machine

7. Draw the finite state machine.

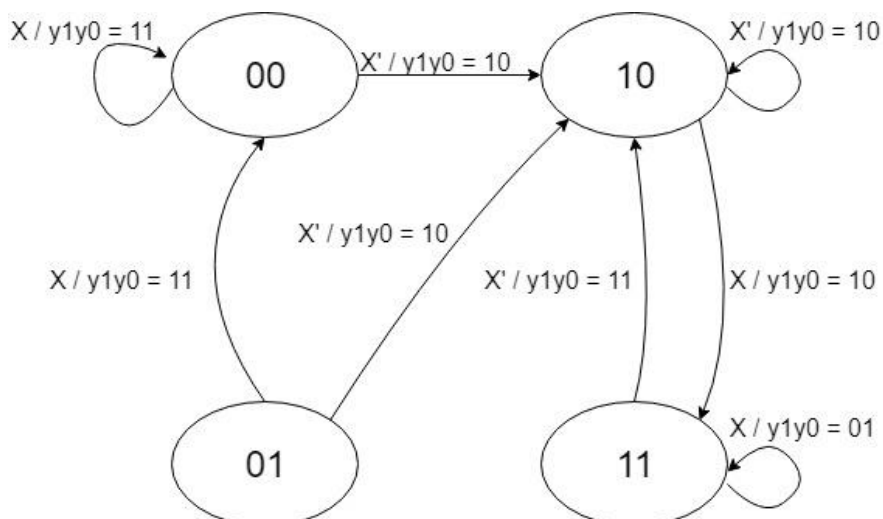

Date: 09.04.2019

Student Names: Salih Can Özçelik / Muhammed Halas

Student IDs: 2016400207 / 2016400228

Group ID: 6

Session ID: 2

Since the initial state is given to be '00', FSM simplifies to this one. (Can't reach state '01'.)

